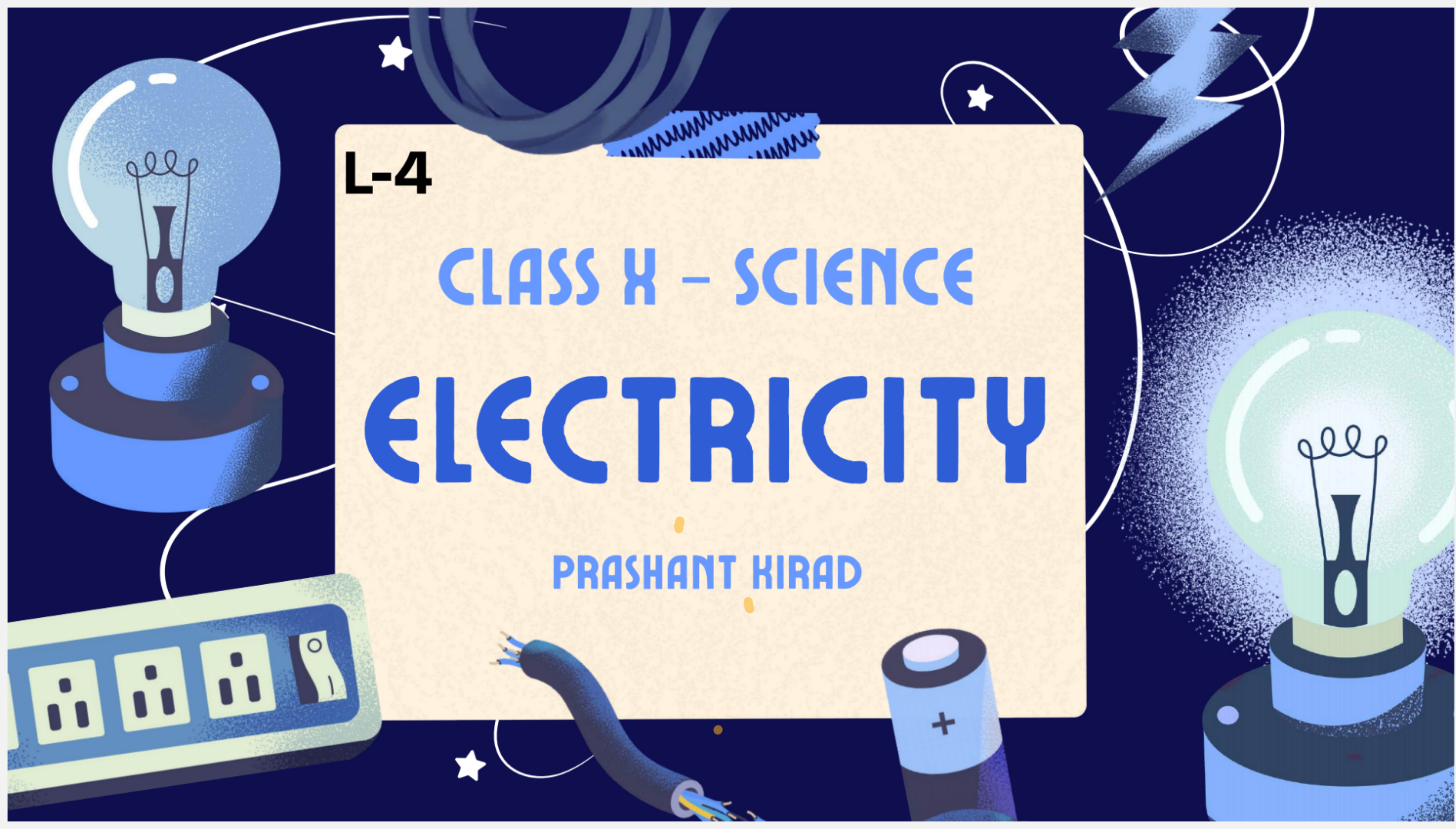


L-4

CLASS X – SCIENCE

ELECTRICITY


PRASHANT KIRAD



Q. Consider the following combinations of resistors: (1 Mark)

The combinations having equivalent resistance $1\ \Omega$ is/are:

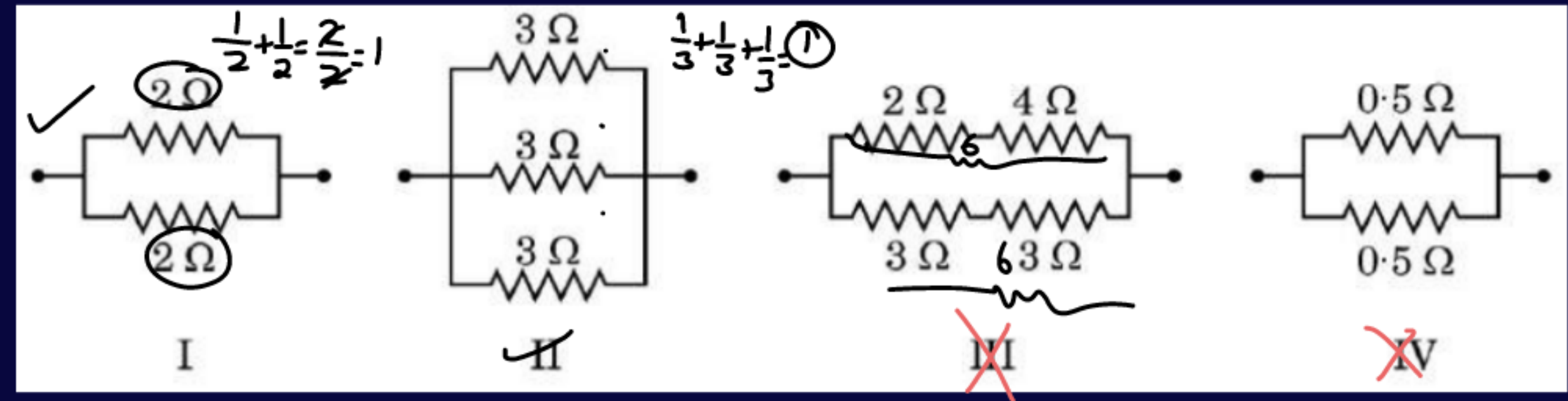- (a) I and IV
- (b) Only IV
- (c) I and II
- (d) I, II and III



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


R_{eq}

$$\frac{1}{0.5} + \frac{1}{0.5} = \frac{2}{0.5}$$

$$= \frac{0.5}{2} = 0.25\ \Omega$$

2Ω 3Ω 6Ω
~~~~~

$R_{min} \rightarrow$


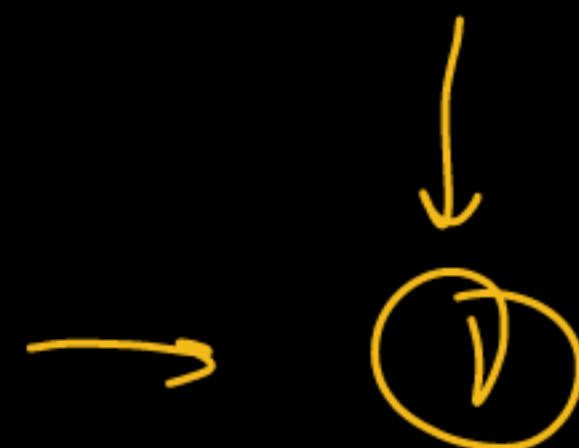


$R_{max} \rightarrow \text{Series}$

$\rightarrow 11\Omega$

**Q.** The image shows a combination of 4 resistors. What is the net resistance between the two points in the circuit?

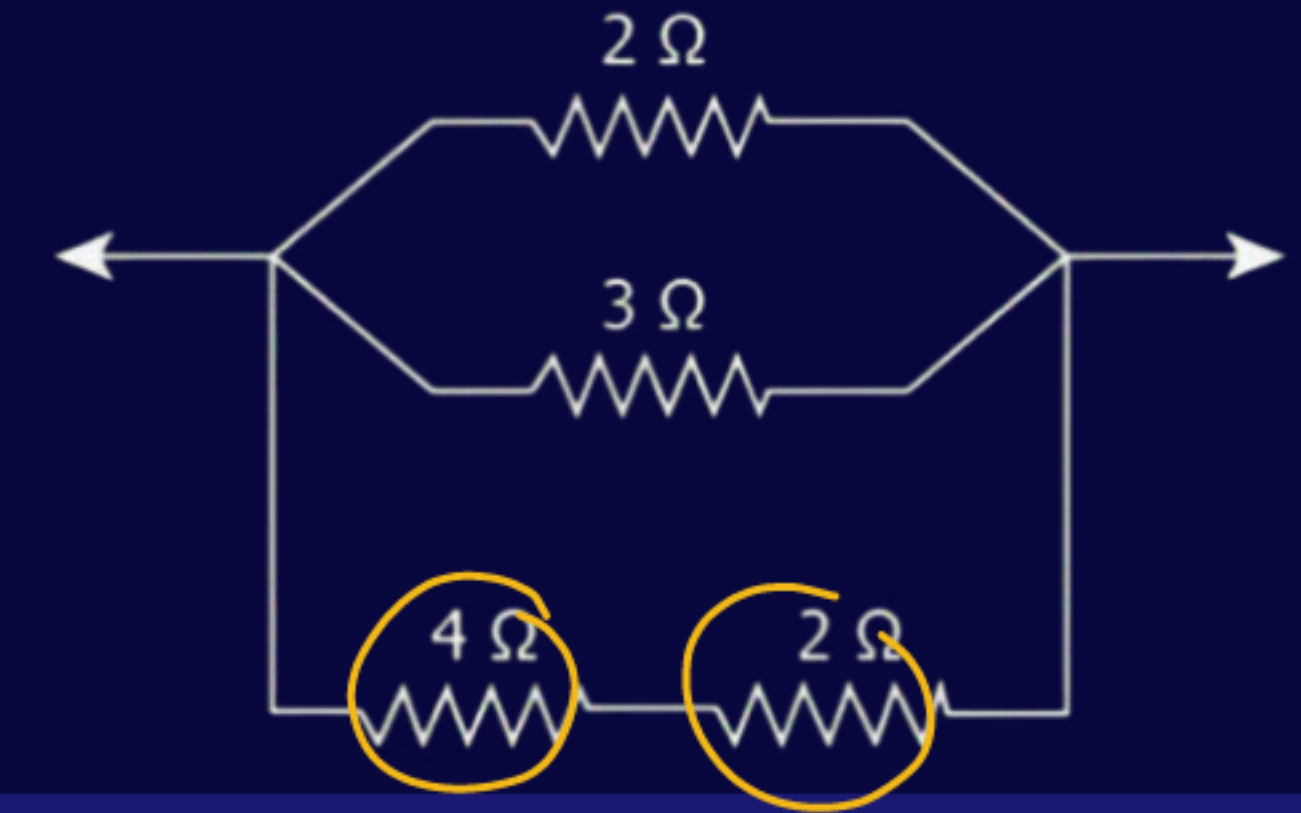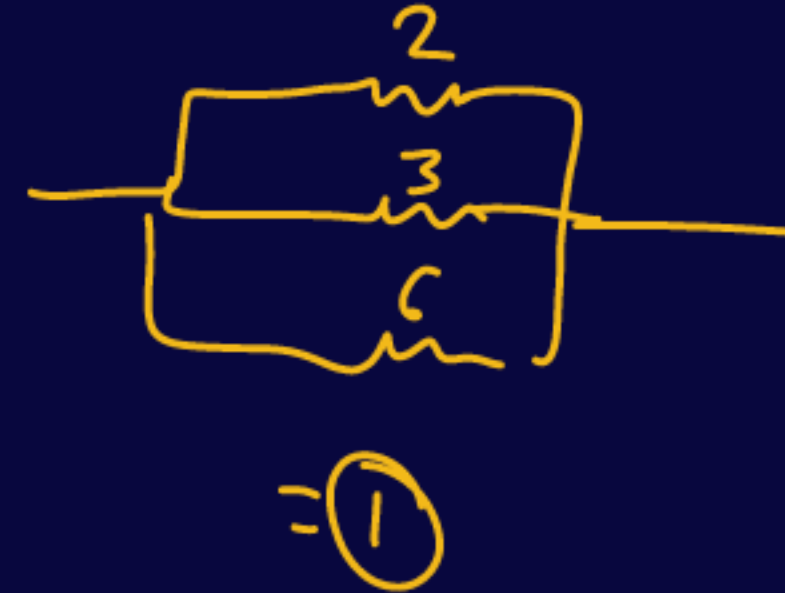
- (a)  $0.5 \Omega$
- (b)  $1.0 \Omega$
- (c)  $1.5 \Omega$
- (d)  $2.0 \Omega$





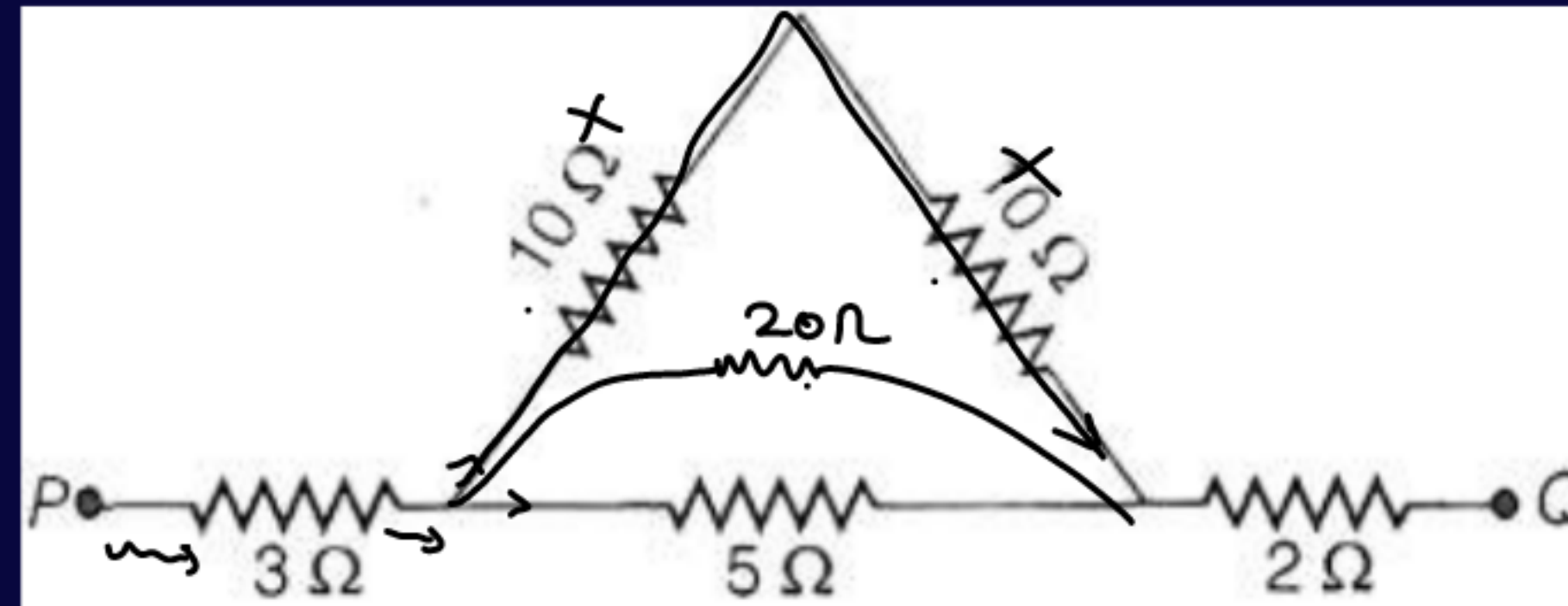**Q. Calculate the equivalent resistance**

$$\frac{1}{20} + \frac{1}{5} = \frac{4+1}{20} = \frac{5}{20} = \frac{1}{4} \Rightarrow 4\Omega$$





$$\begin{array}{c} 3\Omega \quad 4\Omega \quad 2\Omega \\ \hline 9\Omega \end{array}$$



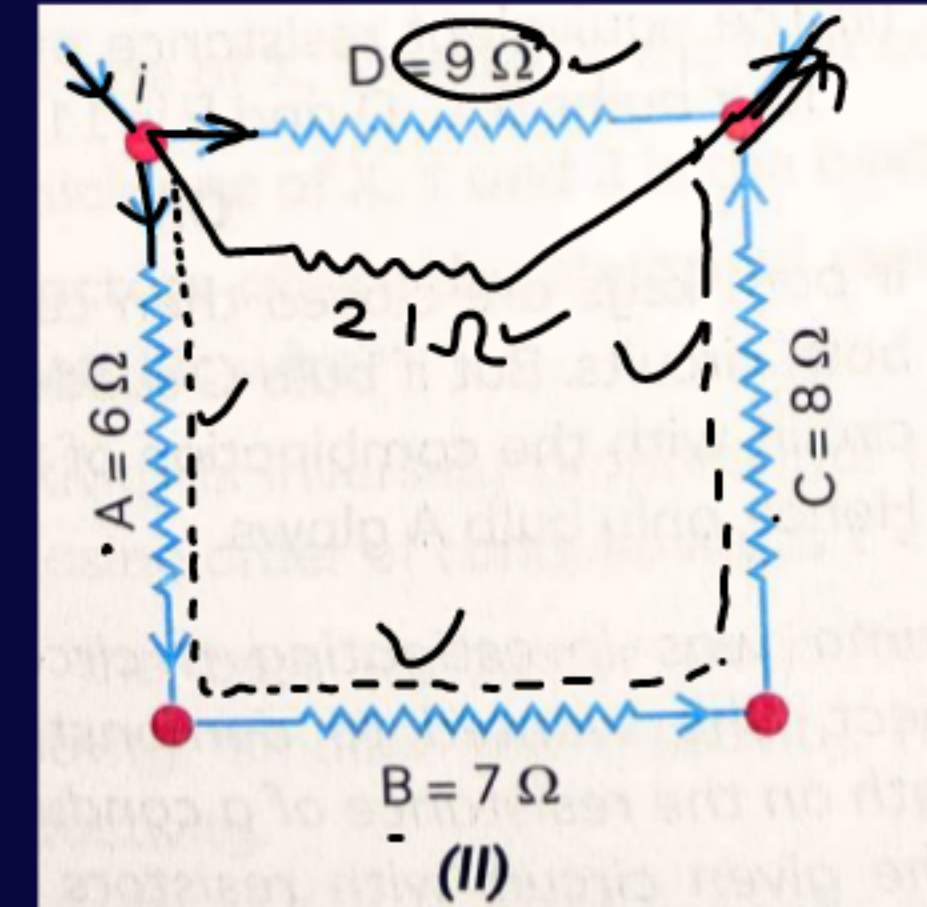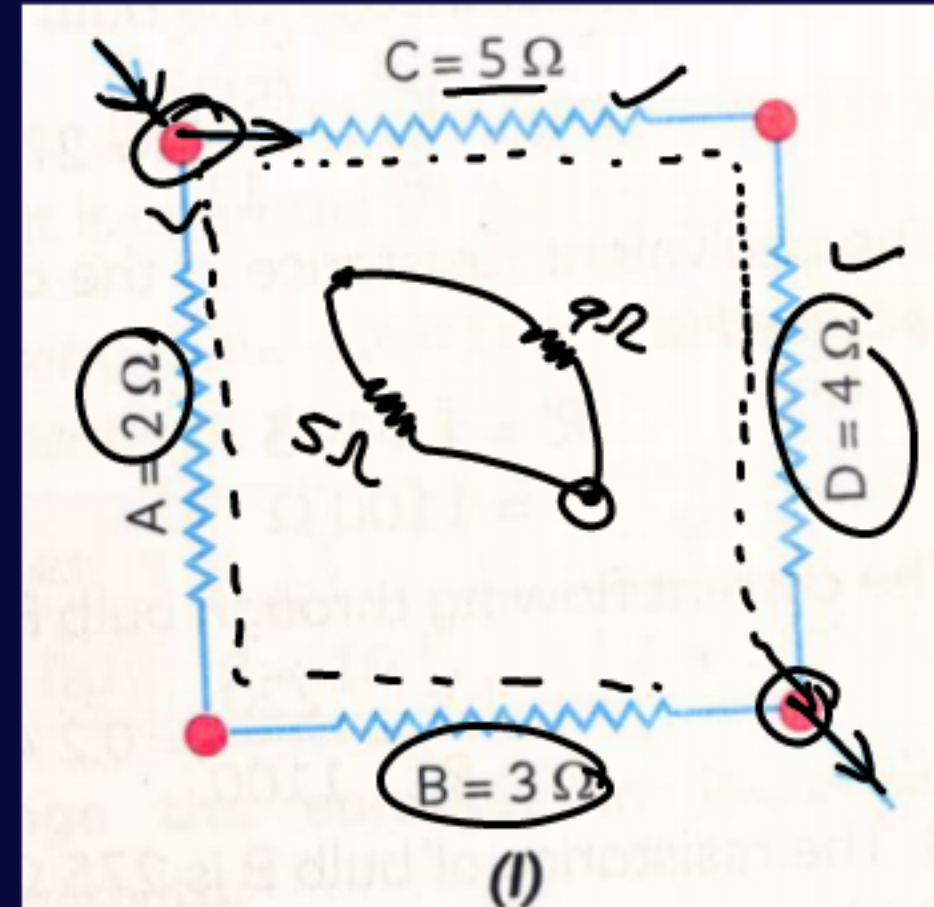**Q. Calculate the total resistance in diagrams (I) and (II).**


$$\begin{aligned} & \frac{1}{4} + \frac{1}{5} \\ &= \frac{14}{45} \\ &= \frac{45}{14} \Omega \end{aligned}$$



$$\frac{1}{4} + \frac{1}{21} = \frac{7+3}{63} = \frac{10}{63}$$

$$\frac{63}{10} \Omega$$

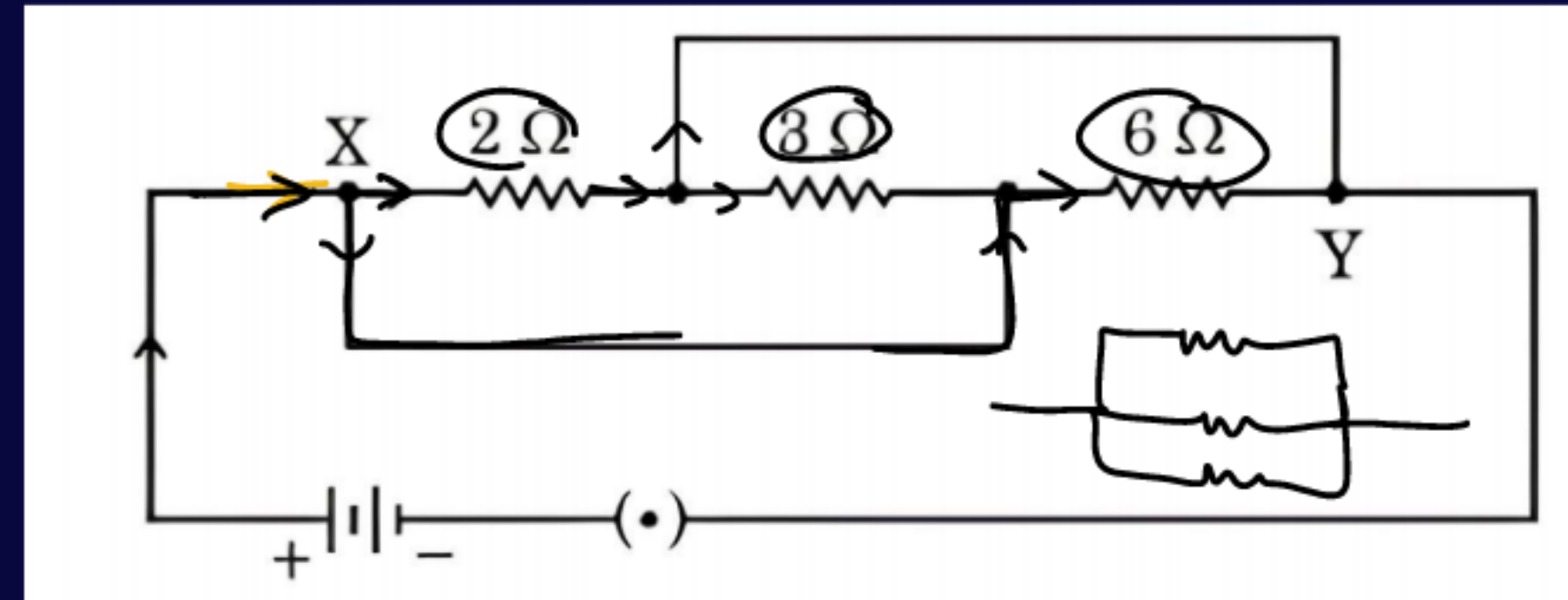**Q.** In the given circuit, the total resistance between X and Y is to be calculated. The circuit contains resistors of  $2\ \Omega$ ,  $3\ \Omega$  and  $6\ \Omega$  connected as shown in the figure. Find the equivalent resistance between X and Y.



## NCERT

**Q.** A piece of wire of resistance  $R$  is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is  $R'$ , then the ratio  $R/R'$  is –

(a)  $1/25$

(b)  $1/5$

(c)  $5$

(d)  $25$



$$\frac{R}{\frac{R}{25}} = 25$$

$$\begin{aligned} \frac{1}{R'} &= \frac{5}{R} + \frac{5}{R} + \frac{5}{R} + \frac{5}{R} + \frac{5}{R} \\ &= \frac{25}{R} \end{aligned}$$

$\frac{R}{25}$

$$R' = \frac{R}{25}$$



NCERT


Q. How can three resistors of resistances  $2\ \Omega$ ,  $3\ \Omega$ , and  $6\ \Omega$  be connected to give a total resistance of (a)  $4\ \Omega$  (b)  $1\ \Omega$ ?



$$R = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2\ \Omega$$



# PK Trick

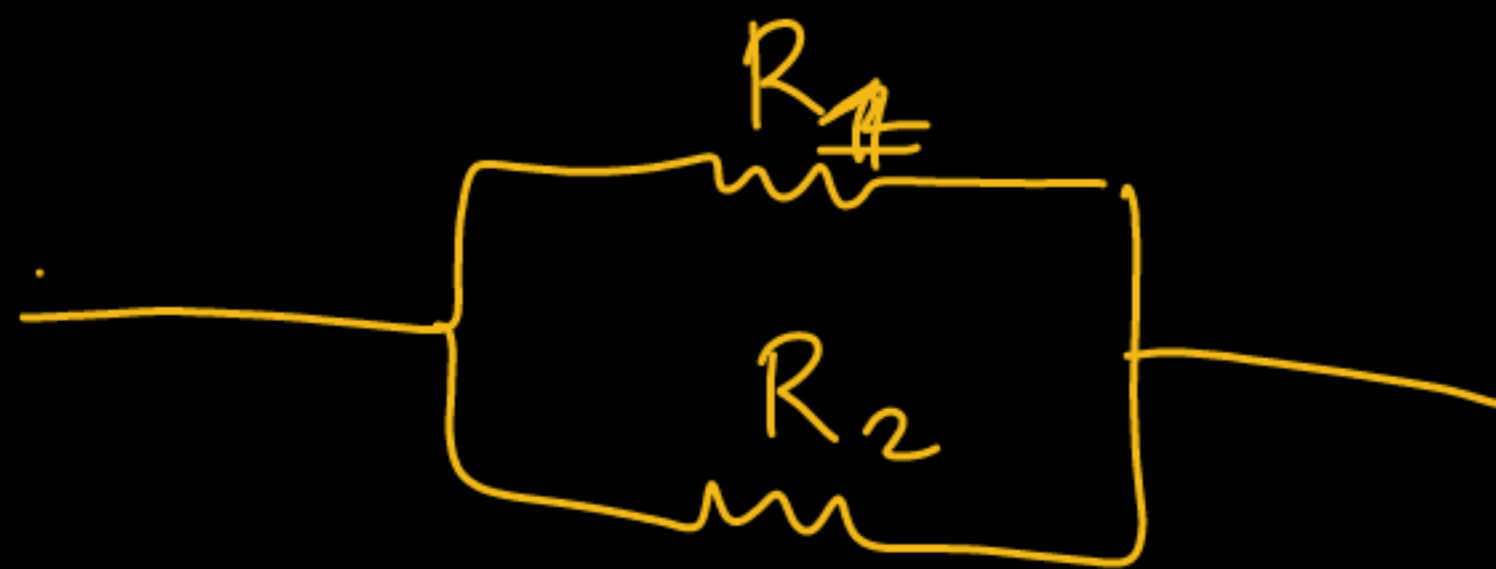

$$R_{net} = \frac{R_1 \times R_2}{R_1 + R_2}$$



NCERT

Q. What is (a) the highest, (b) the lowest total resistance that can be secured by combinations of four coils of resistance  $4\ \Omega$ ,  $8\ \Omega$ ,  $12\ \Omega$ ,  $24\ \Omega$ ?

Series


Parallel



NCERT

$$V_1 = IR$$
$$= \frac{1}{4} \times 4 = 1V$$

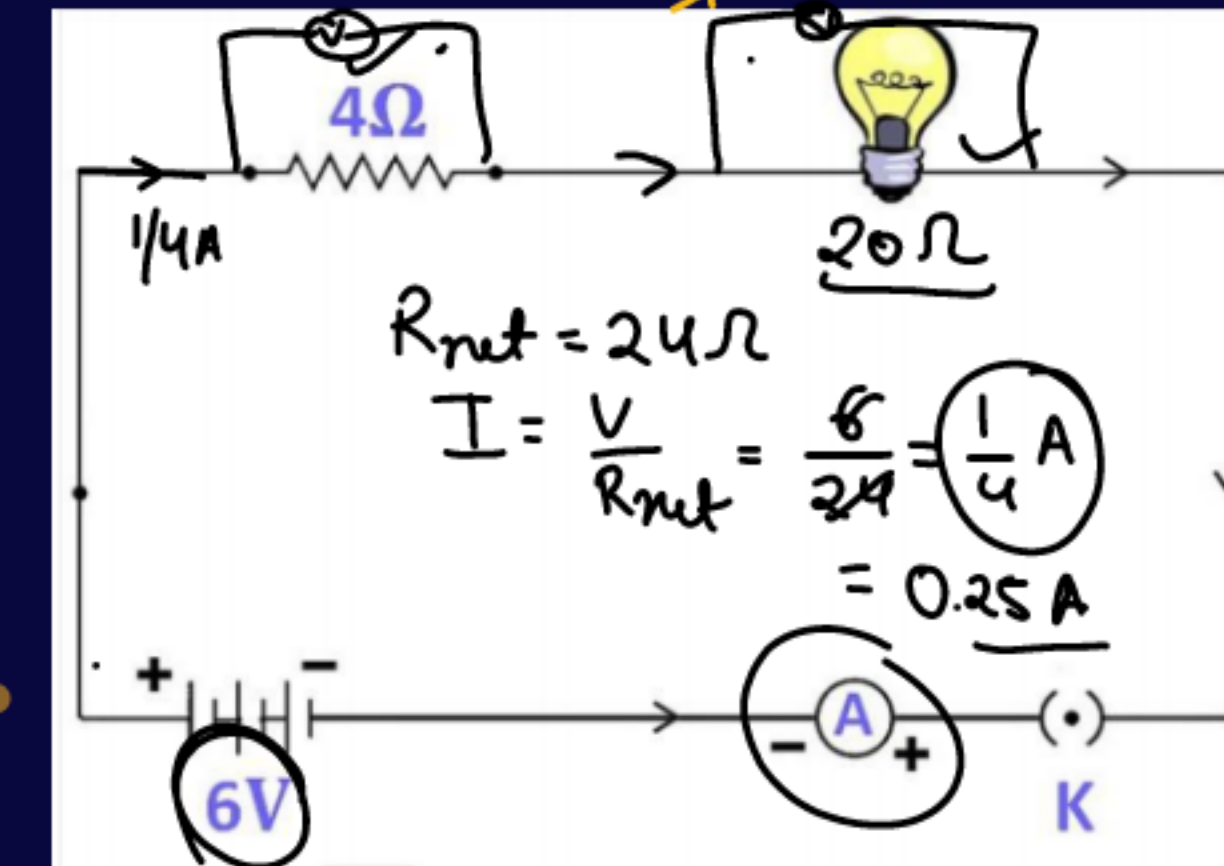- Q. An electric lamp, whose resistance is  $20\ \Omega$ , and a conductor of  $4\ \Omega$  resistance are connected to a  $6\text{ V}$  battery (Fig. 11.9). Calculate
- the total resistance of the circuit,
  - the current through the circuit, and
  - the potential difference across the electric lamp and conductor.



$$\textcircled{1} \rightarrow R_{\text{net}}$$

$$\textcircled{2} \rightarrow \underline{I} = \frac{V}{R_{\text{net}}}$$

$$\textcircled{3}$$




## NCERT

**Q.** Draw a schematic circuit diagram consisting of a battery of three cells of 2 V each, a  $5\ \Omega$  resistor, an  $8\ \Omega$  resistor, a  $12\ \Omega$  resistor, a plug key and an ammeter, all connected in series. Also connect a voltmeter to measure the potential difference across the  $12\ \Omega$  resistor. Calculate the readings of the ammeter and the voltmeter.
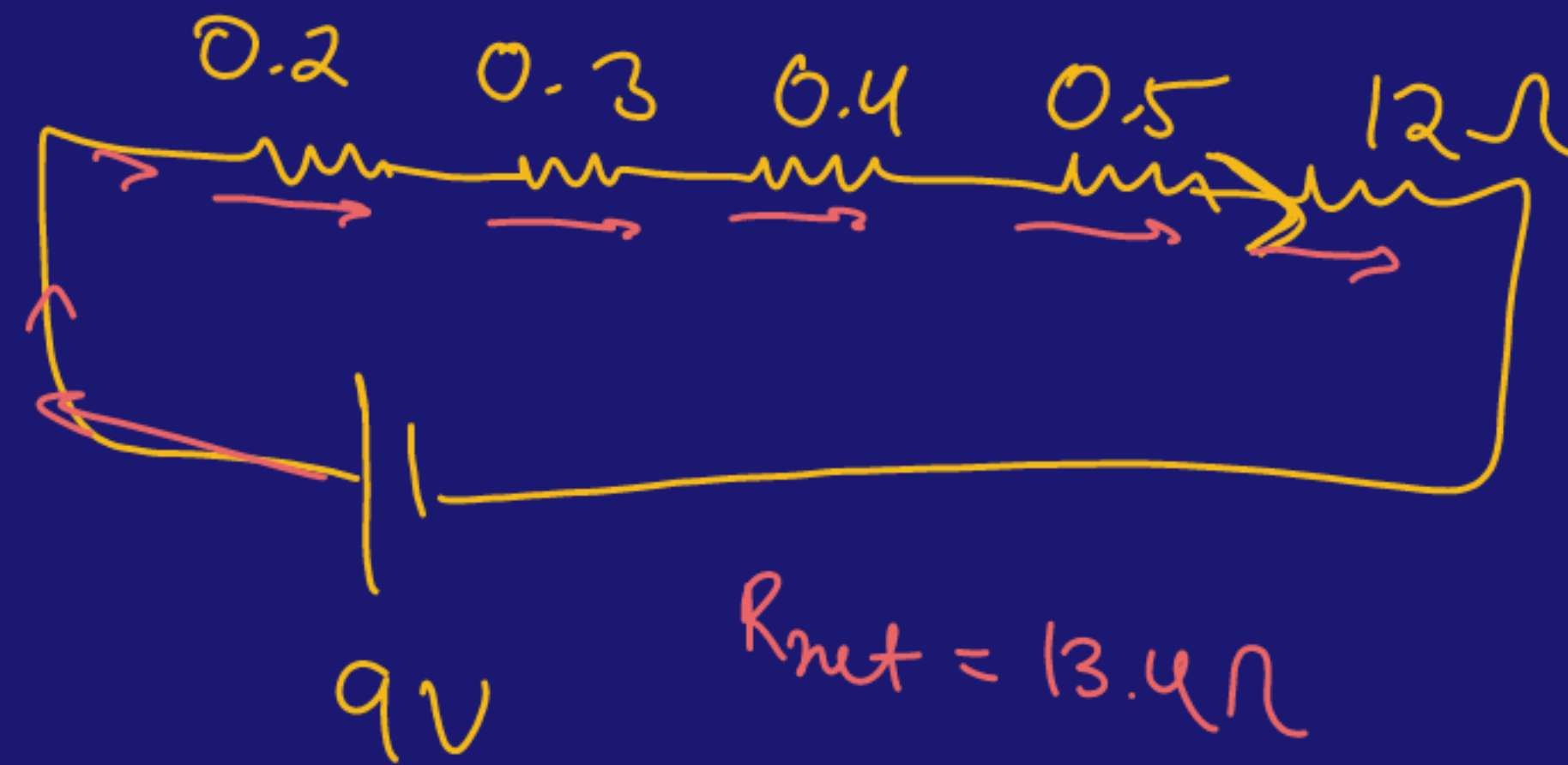
## NCERT

Q. A battery of 9 V is connected in series with resistors of  $0.2\ \Omega$ ,  $0.3\ \Omega$ ,  $0.4\ \Omega$ ,  $0.5\ \Omega$  and  $12\ \Omega$ , respectively. How much current would flow through the  $12\ \Omega$  resistor?



$$R_{\text{net}} = 13.4\ \Omega$$

$$I = \frac{V}{R_{\text{net}}} = \left( \frac{9}{13.4} \right)$$

NCERT


Q. How many  $176\ \Omega$  resistors (in parallel) are required to carry 5 A on a 220 V line?

$$V = 220\text{ V} \checkmark$$

$$I = 5\text{ A} \checkmark$$

$$V = IR$$
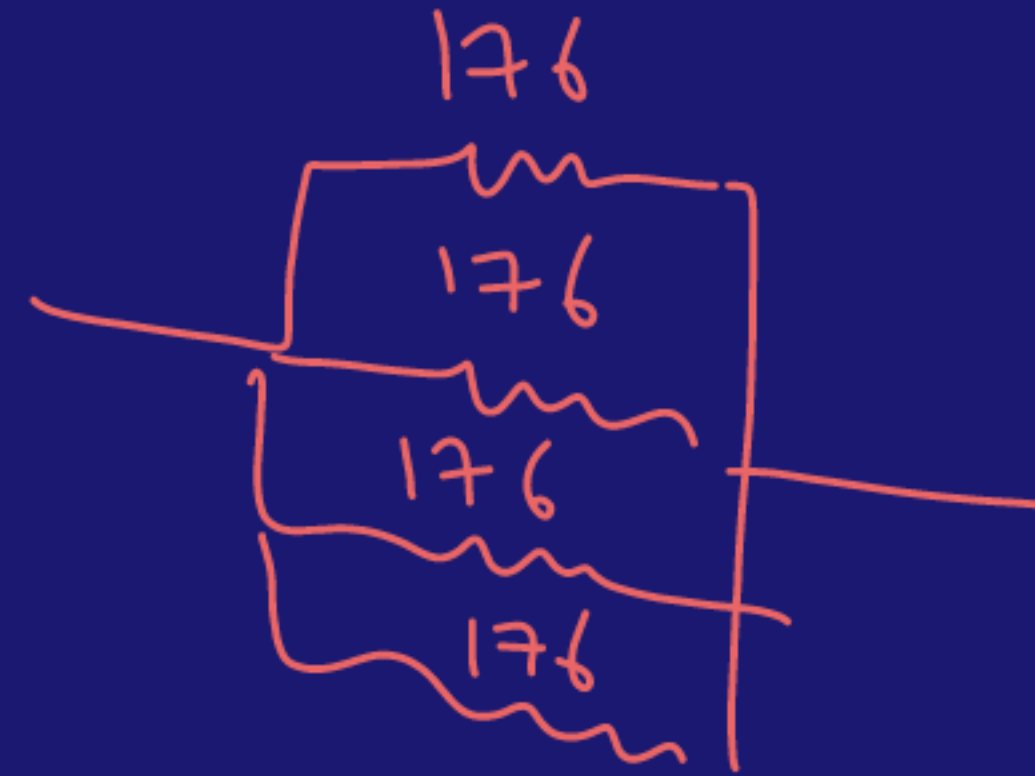
$$R = \frac{V}{I} = \frac{220}{5} = 44\ \Omega$$




$$\begin{aligned} \frac{1}{R_{\text{net}}} &= \frac{1}{176} + \frac{1}{176} + \frac{1}{176} + \frac{1}{176} \\ &= \frac{4}{176} = \frac{1}{44} \Rightarrow 44\ \Omega \end{aligned}$$



**Q. In the given circuit, when the key is closed, determine the following:**

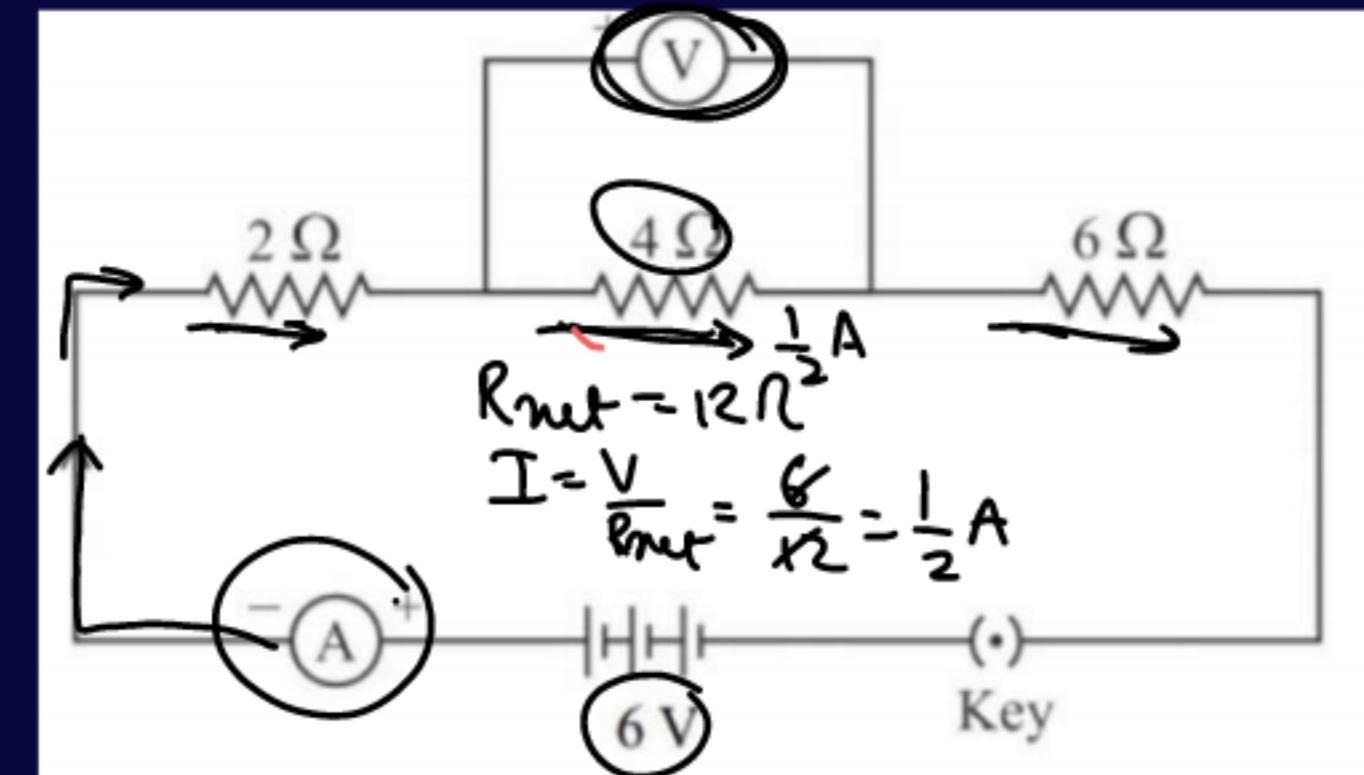- (i) Equivalent resistance of the circuit**
- (ii) Current flowing in the circuit**
- (iii) Reading of the ammeter**
- (iv) Potential difference across the  $4\ \Omega$  resistor**
- (v) Reading of the voltmeter**




**Q. Consider the given electric circuit.**

**Calculate the following:**

**(a) Total resistance of the circuit**

**(b) The electric current drawn from the battery**

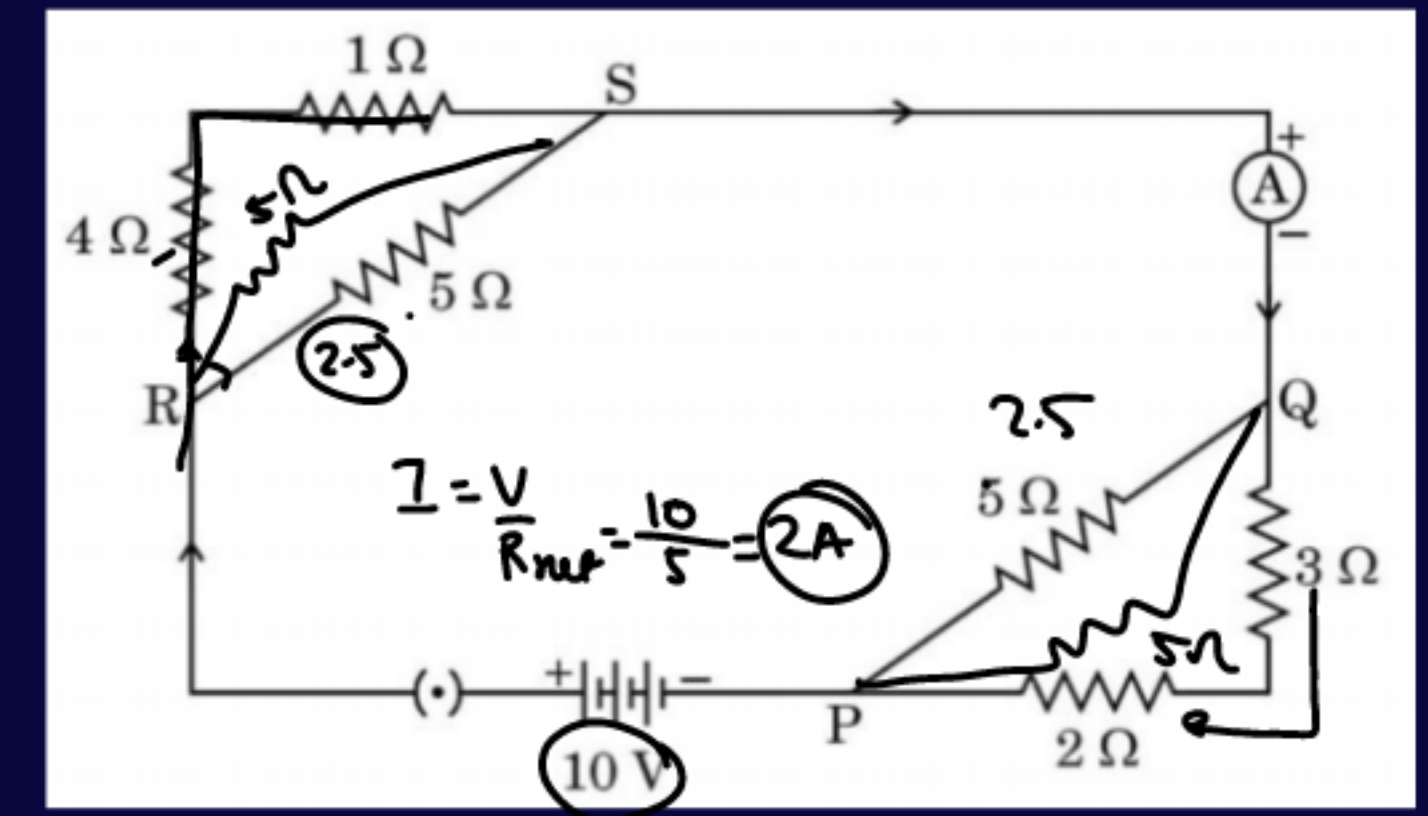
**(c) Potential difference between points P and Q**



**Q.** The given electric circuit is a part of an electrical device. Use the information given in the electric circuit diagram to calculate:

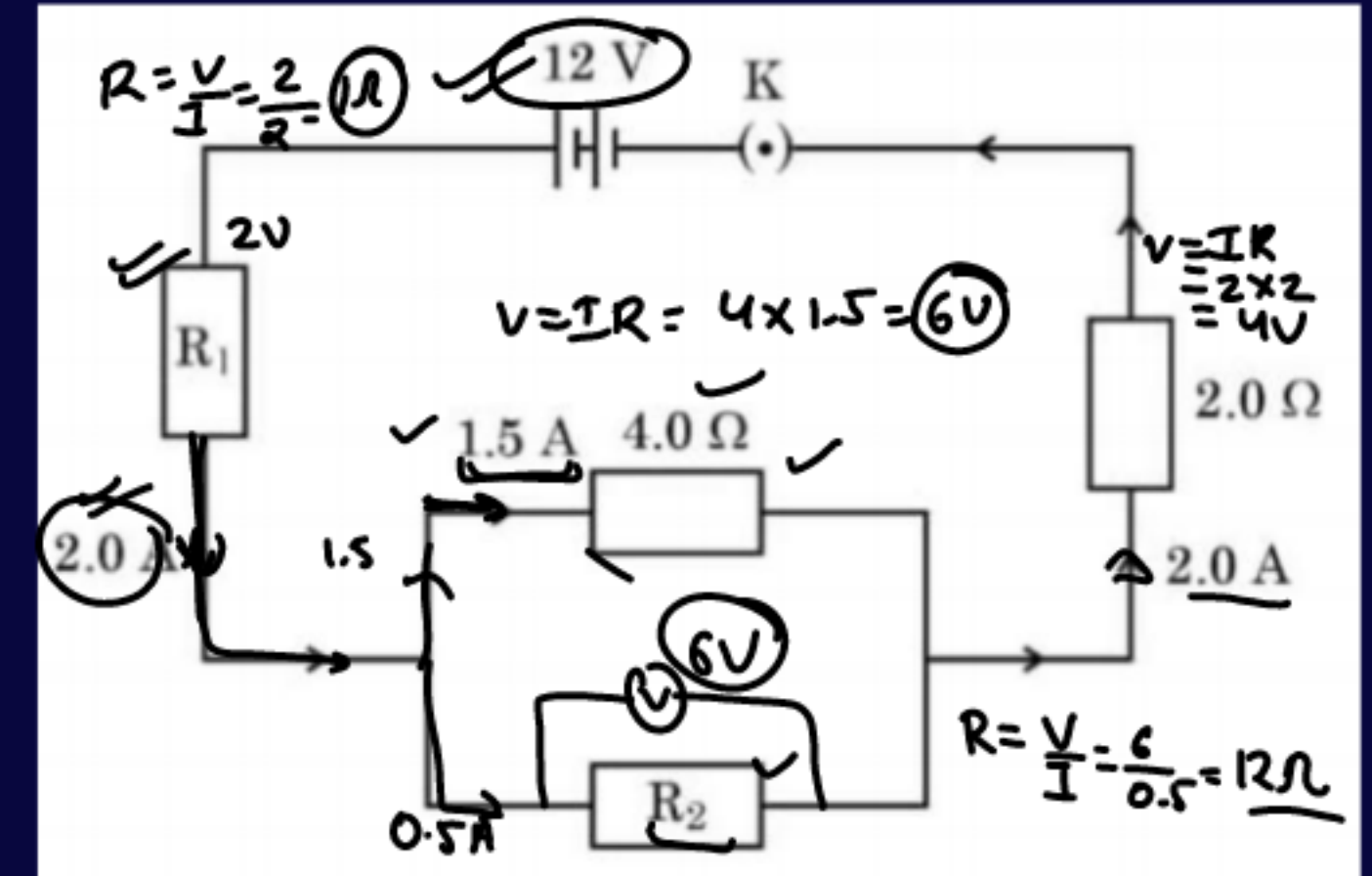- (i) Potential difference across the ends of resistor  $R_2$ .
- (ii) Value of resistor  $R_2$ .
- (iii) Value of resistor  $R_1$ .

Also, write the factors on which resistance of a conductor depends and derive the formula for resistance of a given conductor.





NCERT

HW


**Q.** An electric lamp of  $100\ \Omega$ , a toaster of resistance  $50\ \Omega$ , and a water filter of resistance  $500\ \Omega$  are connected in parallel to a  $220\text{ V}$  source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances, and what is the current through it?

**Q.** Three resistors in a circuit are attached as shown in the figure. The resistances of F and G are  $10\ \Omega$  and  $5\ \Omega$  respectively. The resistance of E is unknown. These resistors are connected to a battery having potential difference  $6\text{ V}$ .

(a) What is the term used to describe such an arrangement of resistors?

(b) What is the resistance of E if  $0.3\text{ A}$  current flows through it?

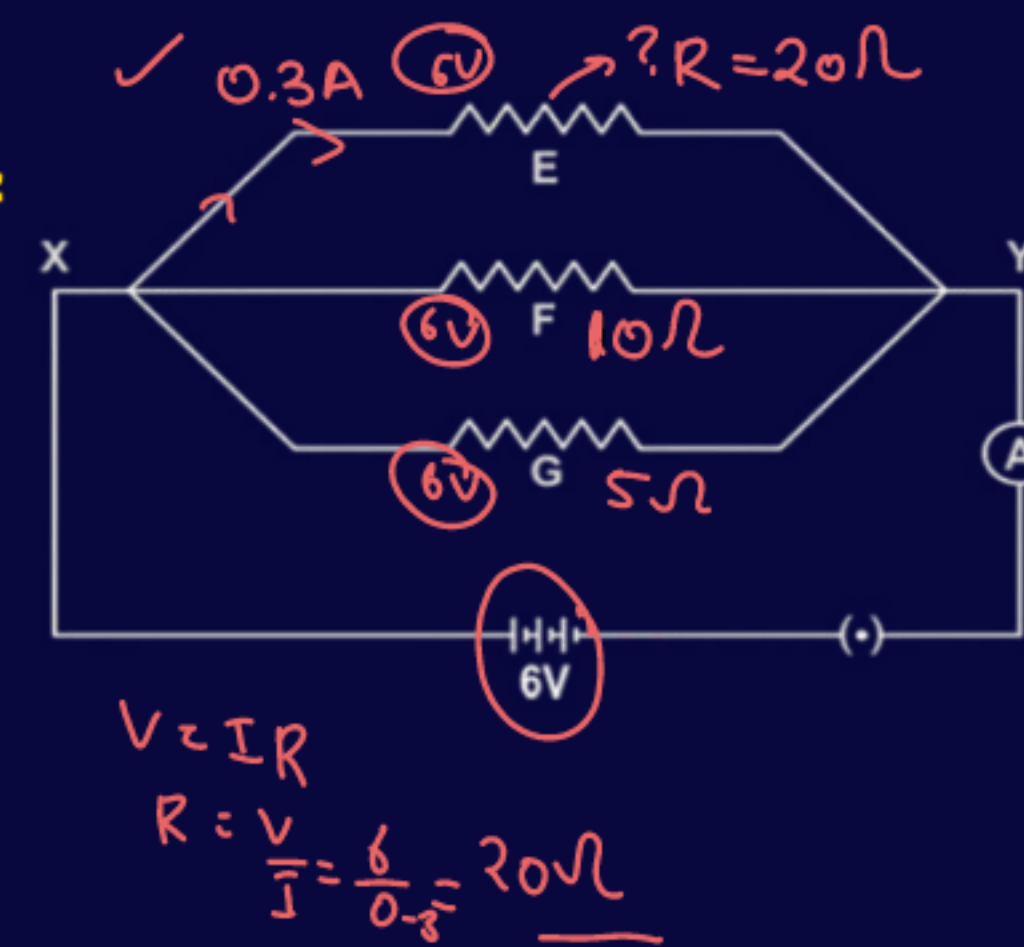(c) What is the total current flowing in the circuit?



$$\frac{1}{R_{\text{net}}} = \frac{1}{20} + \frac{1}{10} + \frac{1}{5}$$


$$= \frac{1+2+4}{20}$$

$$= \frac{7}{20}$$

$$I = \frac{V}{R_{\text{net}}} = \frac{6}{\frac{20}{7}} = \frac{6 \times 7}{20} = \frac{42}{20} = 2.1\text{ A}$$

**Q.** A student has two resistors of  $2\ \Omega$  and  $3\ \Omega$ . She has to put one of them in place of  $R_2$ , as shown in the circuit. The current needed in the entire circuit is exactly  $9\ \text{A}$ . Show by calculation which of the two resistors she should choose.


HW

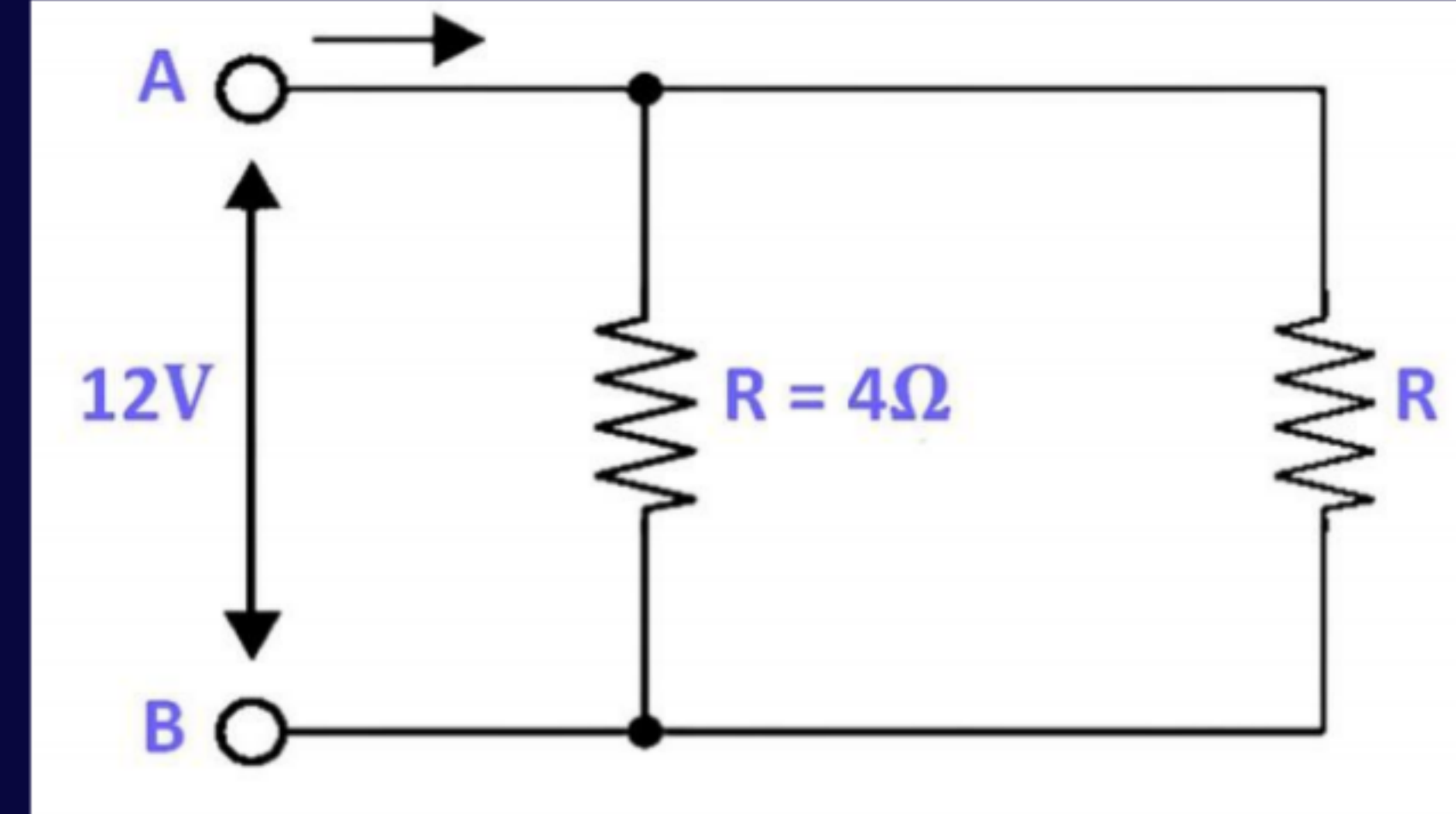


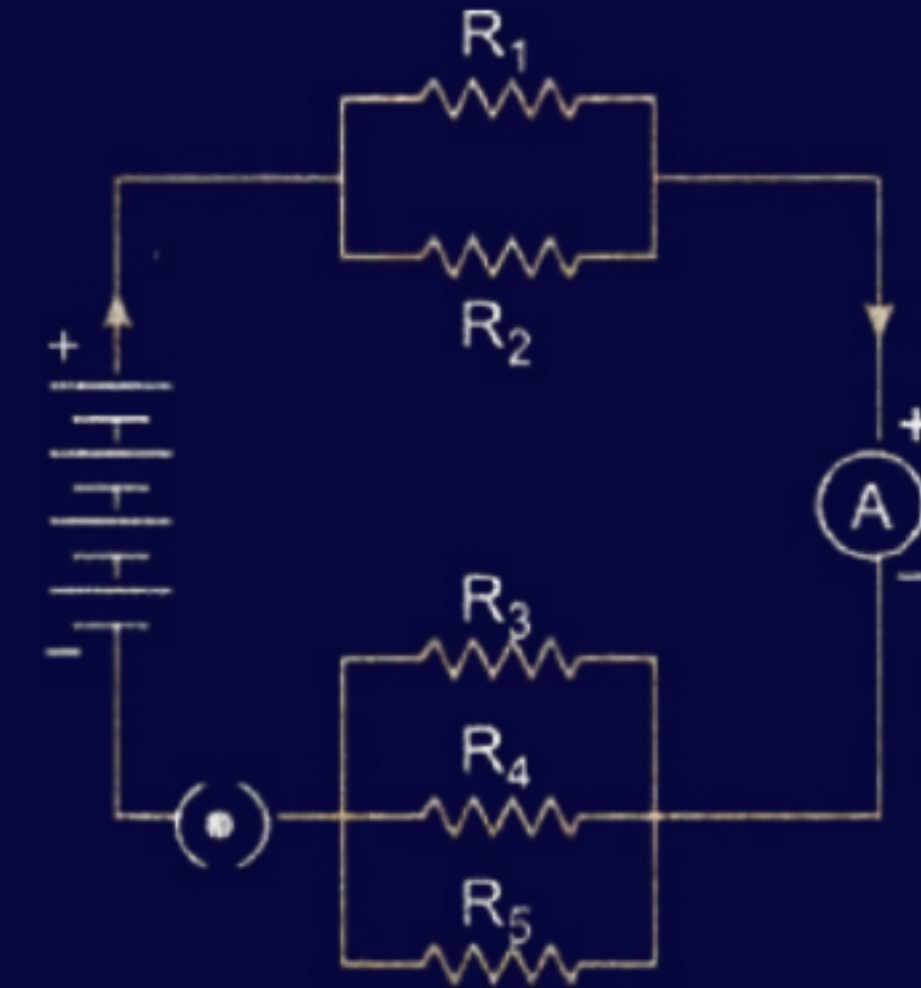
### NCERT

**Q.** If in Fig. 11.12,  $R_1 = 10\ \Omega$ ,  $R_2 = 40\ \Omega$ ,  $R_3 = 30\ \Omega$ ,  $R_4 = 20\ \Omega$ ,  $R_5 = 60\ \Omega$ , and a  $12\text{ V}$  battery is connected to the arrangement. Calculate  
**(a)** the total resistance in the circuit, and  
**(b)** the total current flowing in the circuit.



HW


**Q. Find out the following in the electric circuit given in the figure:**

**(a) Effective resistance of two  $8\ \Omega$  resistors in the combination**

**(b) Current flowing through  $4\ \Omega$  resistor**

**(c) Potential difference across  $4\ \Omega$  resistance**

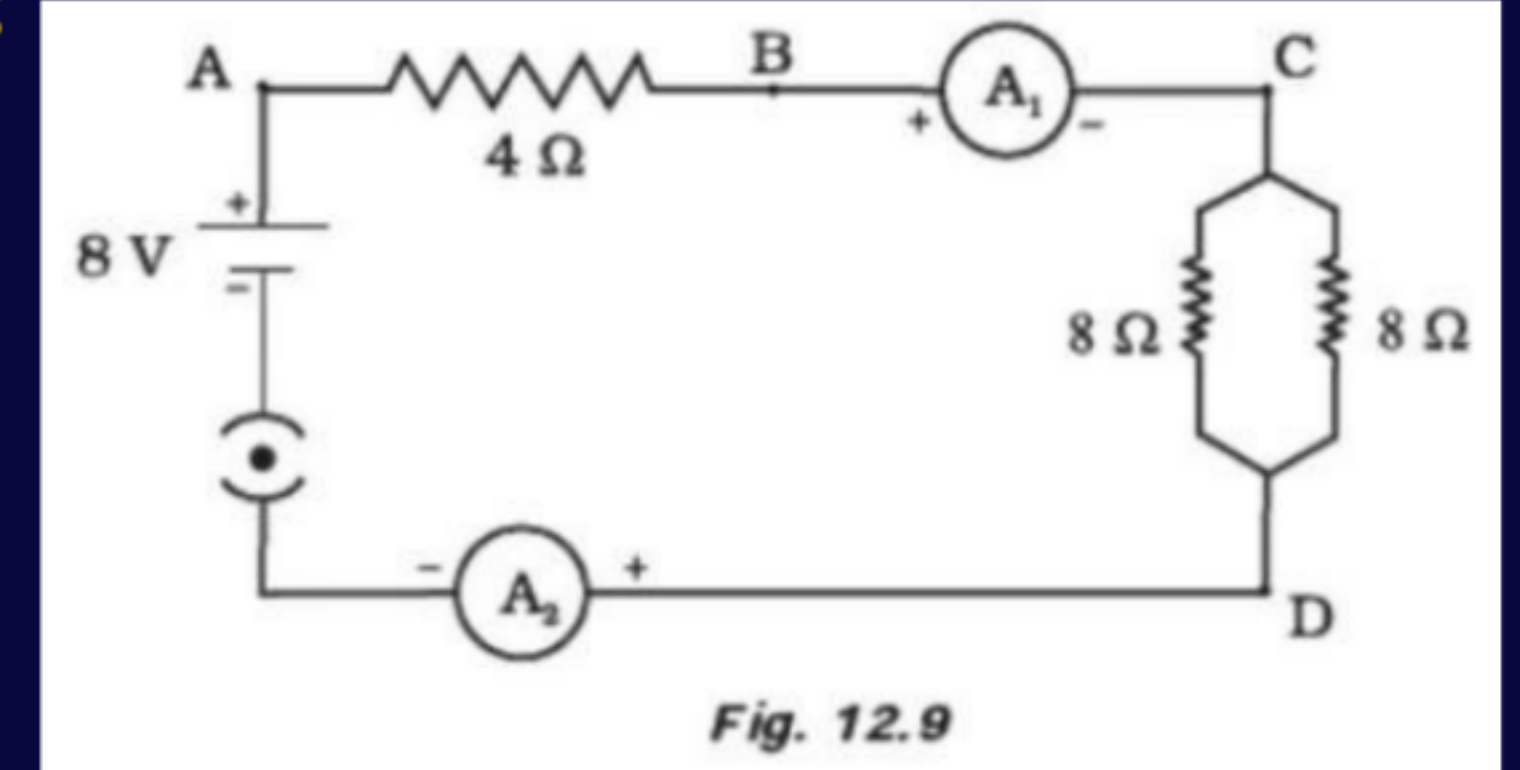**(d) Difference in ammeter readings, if any.**




HW

**Q. Four resistors, a voltmeter and a battery are connected in a circuit as shown below.**

**(A) What is the net resistance in the circuit?**

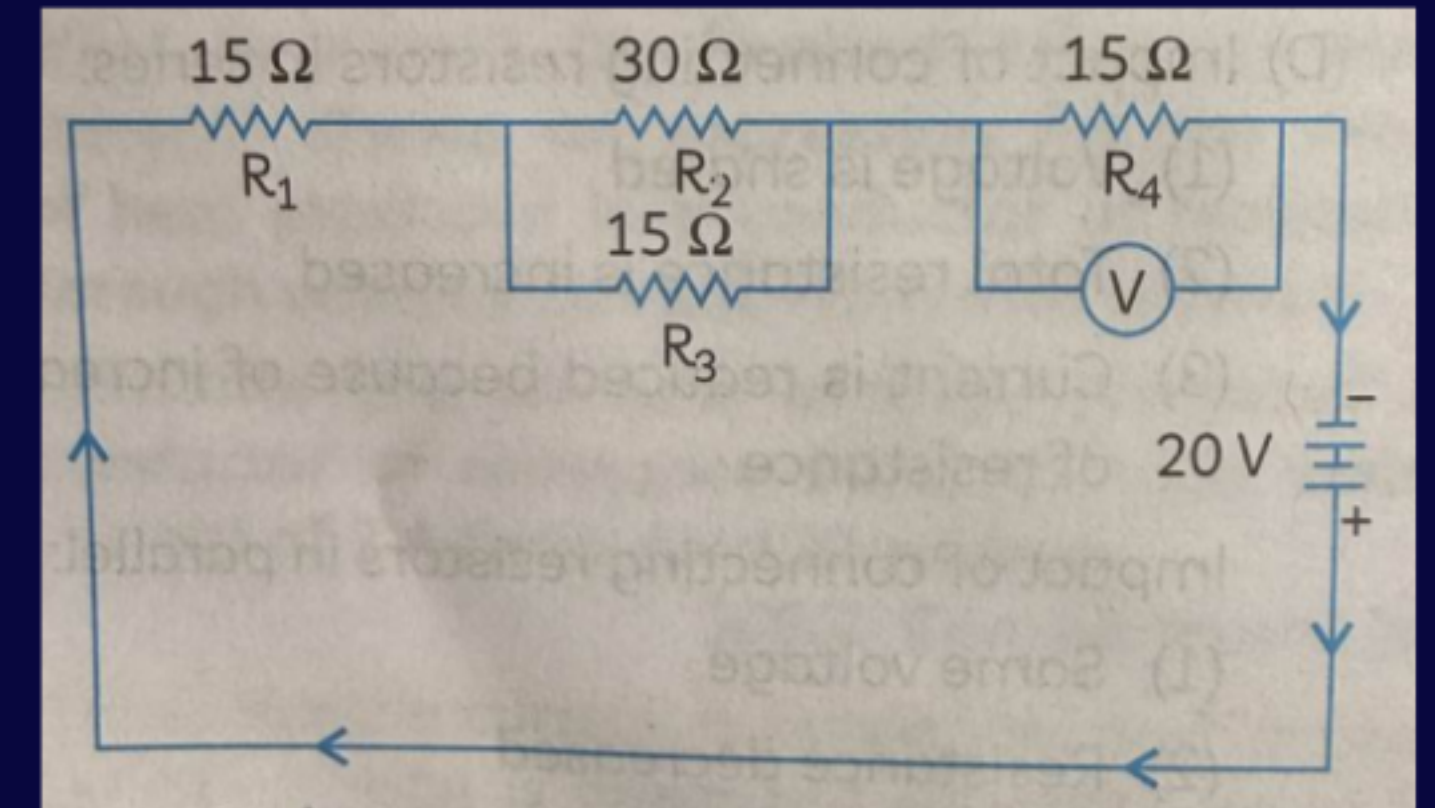**(B) How much potential difference will the voltmeter connected across resistor  $R_4$  measure?**



HW



**Q.** The circuit in the figure has resistors in series and parallel.


**(A)** State two factors that affect the resistance of a resistor.

**(B)** X and Y are meters. Identify X and Y and the electrical property that each meter measures.

**(C)** (i) Calculate the equivalent resistance in the circuit.

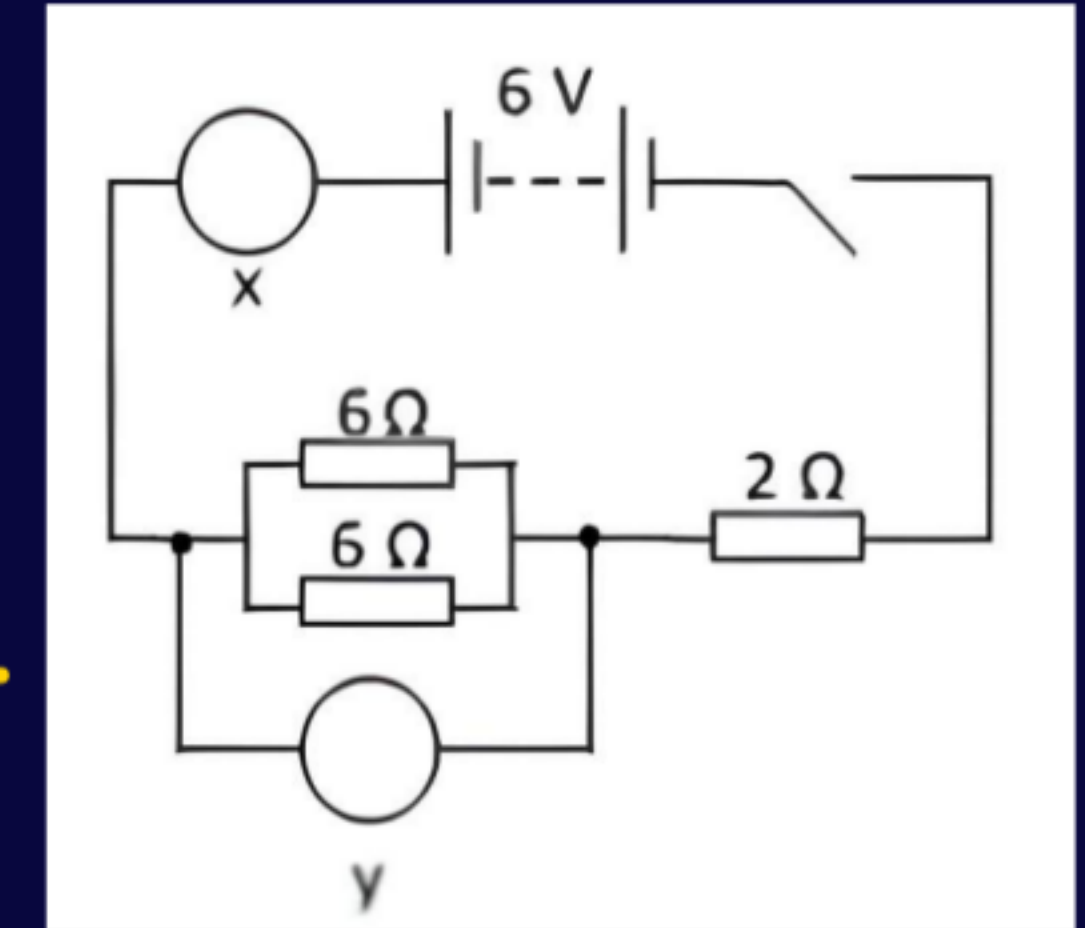(ii) Using your answer, calculate the current in the circuit. State the unit.

**(D)** Explain the impact of connecting resistors in series and connecting resistors in parallel on the resistance of a simple circuit.



Handwritten text:  $11\Omega$